

CS5120 00

GCD Engine

黃稚存



國立清華大學
資訊工程學系

HW 01


Description

- Calculate the greatest common divisor (GCD) of two 8-bit positive integers
- Using a START signal to load inputs
- Generate a DONE signal to indicate the result
- Assert an ERROR signal when one or more inputs are zero


IO Specification

- Inputs:
 - ◆ *CLK*: clock source
 - ◆ *RST_N*: reset (low active)
 - ◆ *START*: to trigger the calculation
 - ▣ A one-cycle pulse to indicate the valid input numbers
 - ◆ *A*, *B*: two 8-bit input numbers
- Outputs:
 - ◆ *Y*: the result
 - ◆ *DONE*: to indicate the valid output with one-cycle pulse
 - ◆ *ERROR*: to indicate an error
 - ▣ 0: normal result
 - ▣ 1: invalid when $A = 0$ or $B = 0$


Primary IOs and Block Diagram

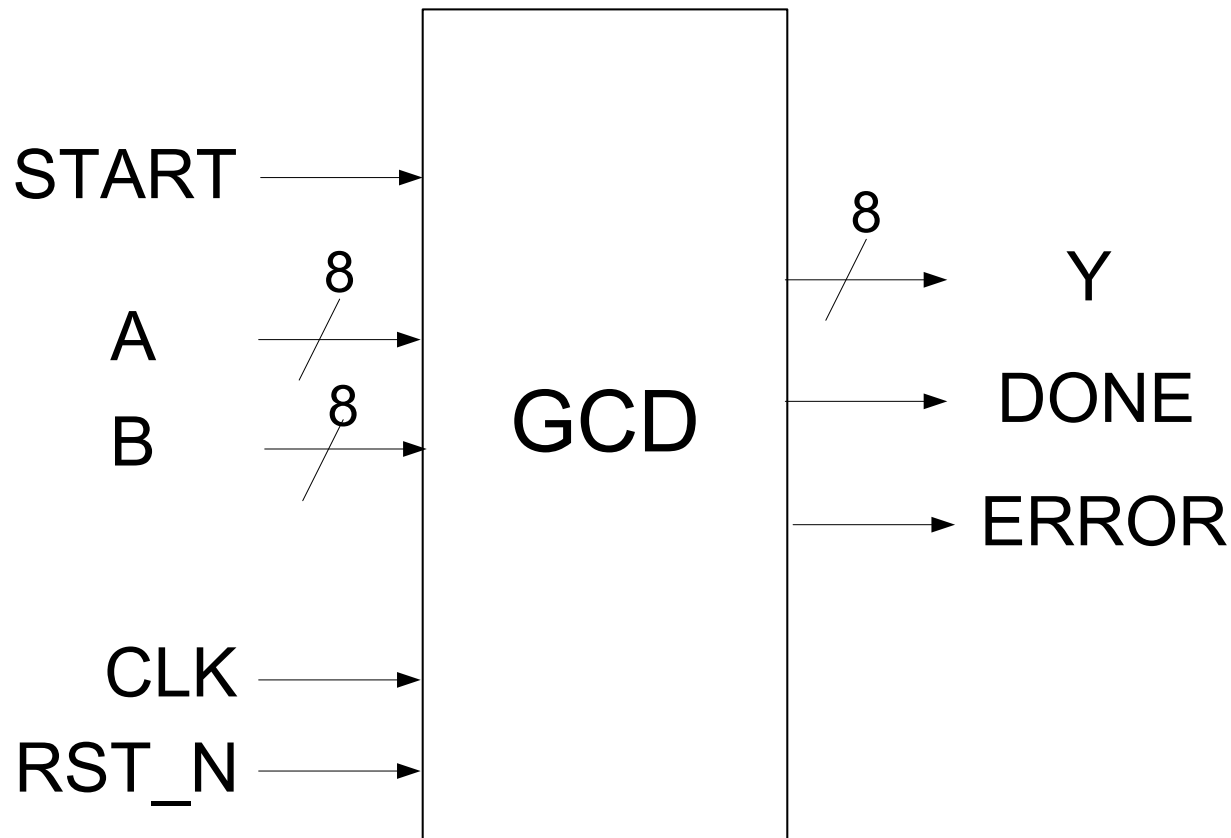


Finite State Machine (for Control)

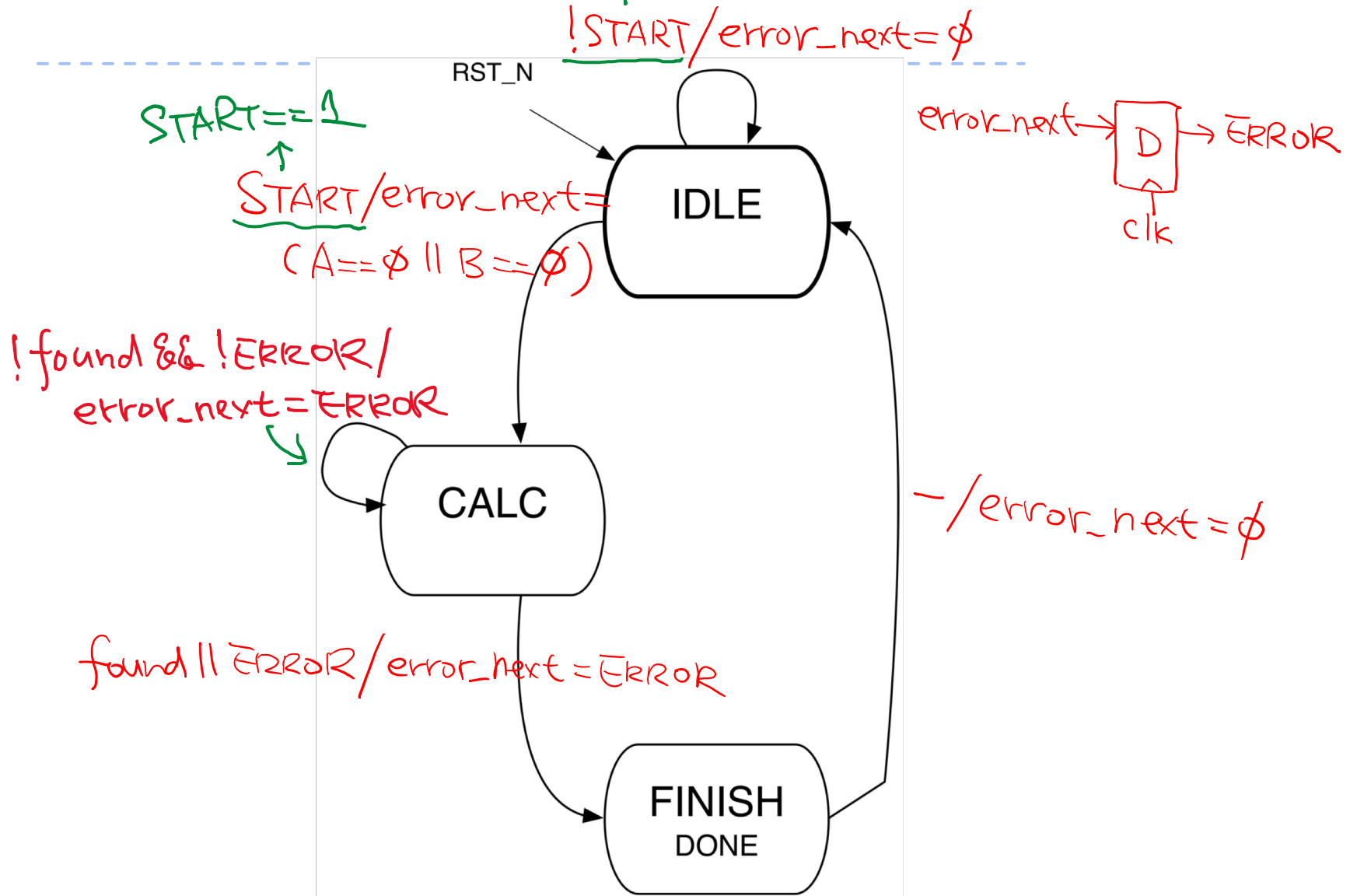


Timing Diagram – Normal Operation

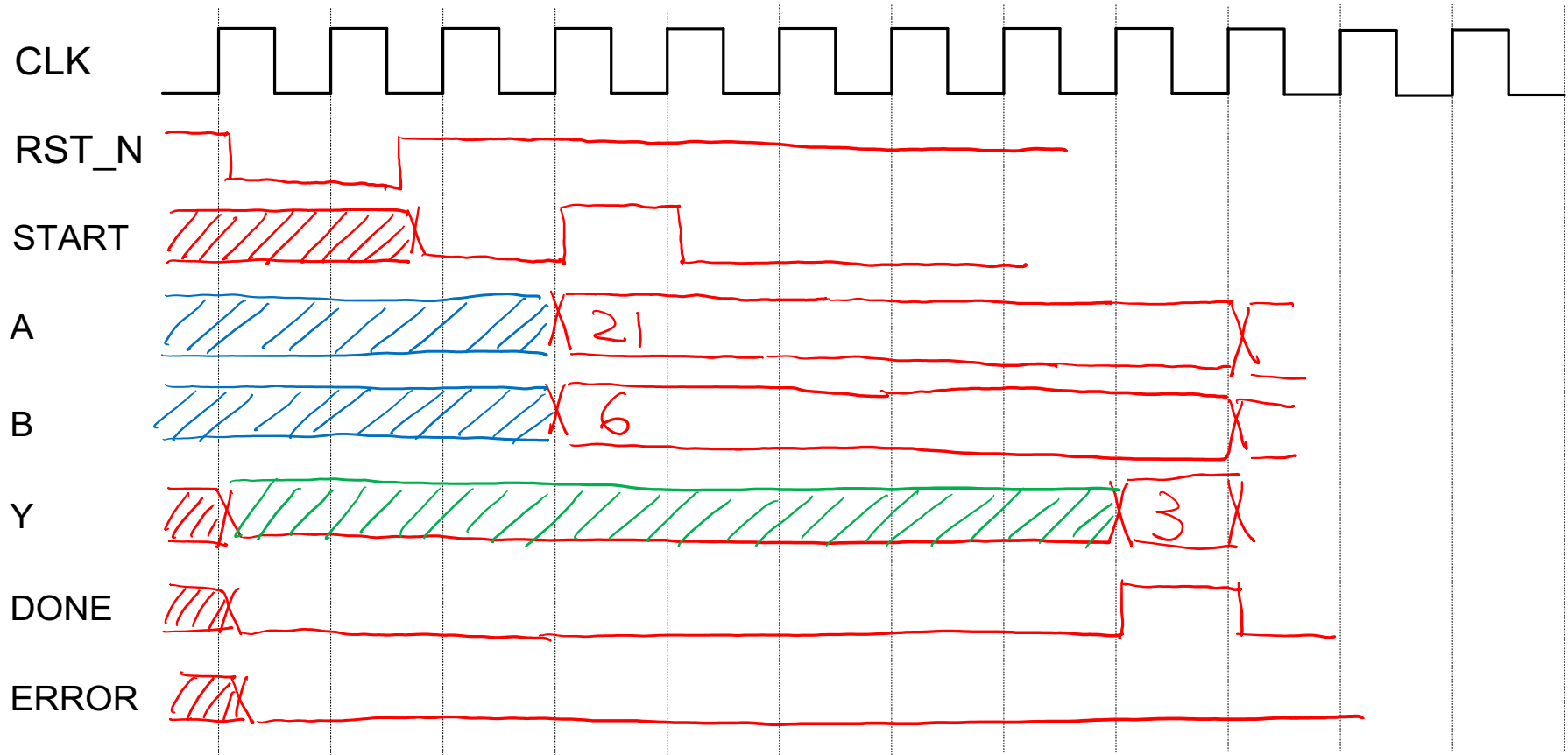

Timing Diagram – Error

 

Overall Architecture (Block Diagram)

 

$\text{Swap} = (\text{reg_b} > \text{reg_a}) ? 1'b1 : \phi;$

$\text{found} = (\text{reg_a} == \text{reg_b} \parallel A == B) ?$

$1'b1 : \phi;$

Design Procedure

- Start with spec, primary IOs, and block diagram
- Design the overall architecture
- Specify finite state machine(s), data path, and internal signals
- List the timing diagrams of major operations
- Verilog coding
- Prepare comprehensive test environment for efficient debugging

Guideline of Design Procedure

- Prepare the block diagram and FSM carefully
- Try to symbolize every condition for
 - ◆ State transitions
 - ◆ Mode selection for datapath
- FSM: the simpler the better
 - ◆ One single state can take multiple cycles
 - ◆ States can be nested
- ◆ Design should be done before Verilog coding
- There is no one BEST style for every design
 - ◆ State arrangement
 - ◆ Naming convention